

Reference Design

**EBC10049**



**iW1760-00 for 19.5V 0.6A  
12W Ultrabook™ Travel Adapter Design**

# **iW1760-00 for 12W Ultrabook™ Travel Adapter Design** **(AC Input 90 - 265V<sub>AC</sub> Output 19.5V 0.6A)** **EBC10049**

1.0. Introduction .....	3
2.0. Design Features .....	3
3.0. Design Specification .....	4
4.0. Schematic .....	5
5.0. PCB Layout.....	5
6.0. Bill of Materials .....	6
7.0. Transformer Drawing .....	7
8.0. Performance .....	8
8.1. Regulation, Ripple and Efficiency .....	8
8.2. Conducted EMI .....	8

## 1.0 Introduction

This document provides a reference design for a universal input, 19.5V 0.6A isolated flyback power supply for ultra-small, 12W Ultrabook travel adapters. This design uses the iW1760-00. This document contains the complete specification for the power supply, a detailed circuit diagram, an entire bill of materials required to build the power supply, a drawing of the power transformer, and test data of the most important performance.



Figure 1.1 PCB Top View

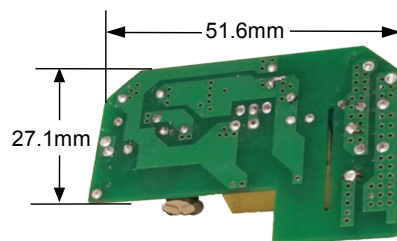


Figure 1.2 PCB Bottom View


## 2.0 Design Features

- AC input range: 90 – 265V<sub>AC</sub>
- DC output: 19.5V, 0.6A
- 82W peak power for 0.2ms every 10ms
  - » Supports Intel Turbo Boost mode
- < 50mW no-load standby power consumption
- Maximum ripple voltage < 380mV<sub>P-P</sub>
- PrimAccurate™ primary-side sensing
  - » Eliminates opto-isolator
  - » Reduces BOM
  - » Improves line voltage surge protection
- Tight over voltage protection

### 3.0 Design Specification

The table below represents the minimum acceptable performance of the design.

Description	Symbol	Min	Typ	Max	Units	Comment
<b>Input</b>						
Voltage	$V_{IN}$	90		265	$V_{AC}$	2 Wire
Frequency	$f_{LINE}$	47	50/60	63	Hz	
No-load input power (230V <sub>AC</sub> )				50	mW	
<b>Output</b>						
Output voltage	$V_{OUT\_CV}$	18.5	19.5	20.5	V	Measured at end of output cable
Output current	$I_{OUT\_CV}$		0.6	4.2	A	4.2A (turbo mode) for 0.2ms every 10ms
Output ripple voltage	$V_{RIPPLE}$			380	mV <sub>P-P</sub>	Measured at end of cable $I_{OUT}=0.6A$ @ $T_A=25^{\circ}C$ 20MHz bandwidth
<b>Total Output Power</b>						
Continuous output power	$P_{OUT}$		12	82	W	82W (turbo mode) for 0.2ms every 10ms
Over-current protection	$I_{OUT\_MAX}$			0.8	A	Auto-restart
Active mode efficiency	$\eta$	85			%	Measured at end of cable $V_{IN}=120V_{AC}$ and $230V_{AC}$ ( $T_{AMB}=25^{\circ}C$ )
<b>Environmental</b>						
Conducted EMI		Meets CISPR22B/EN55022B				
Safety		Designed to meet IEC950, UL1950 Class II				
Ambient temperature	$T_{AMB}$	0		45	°C	Free convection, sea level

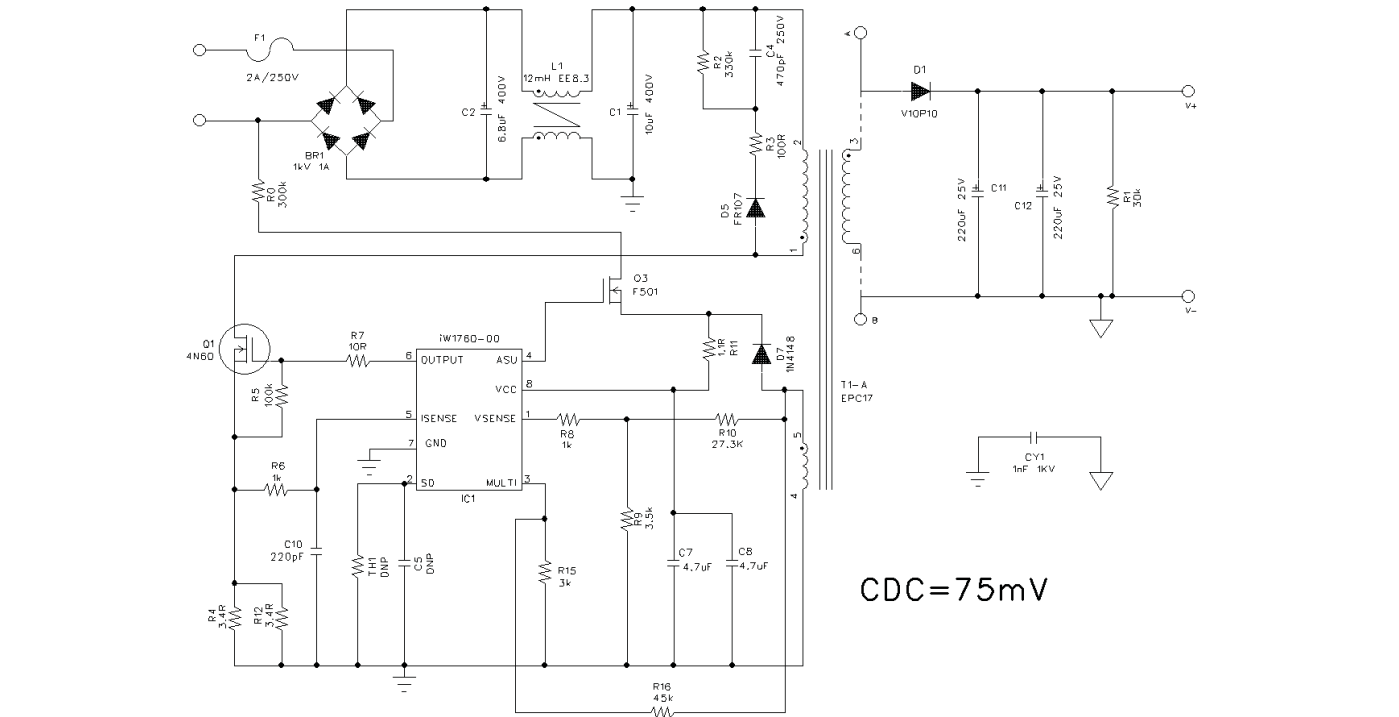

*Figure 4.1 Design Schematic*

## 5.0 PCB Layout

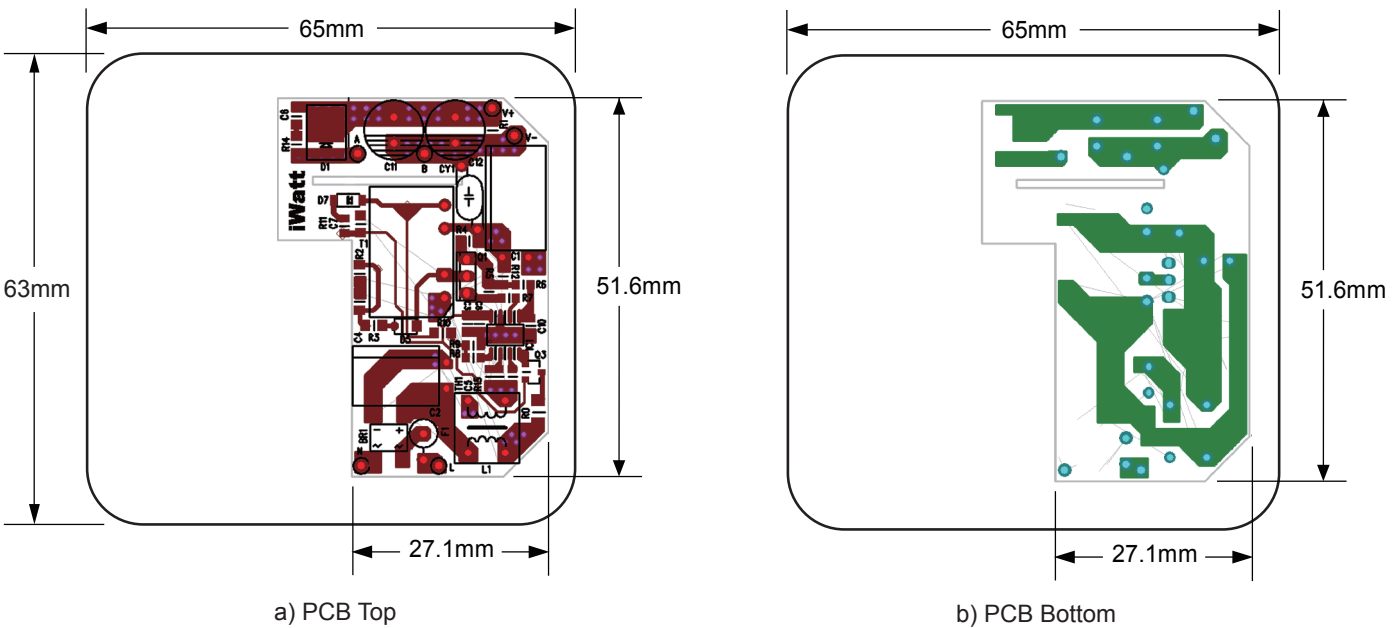



Figure 5.1 PCB Layout 51.6 mm x 27.1 mm

## 6.0 Bill of Materials

Item	Qty.	Ref.	Description
1	1	IC1	IC controller, iW1760-00
2	1	F1	Fuse, 250V, 2A, fast
3	1	L1	CM choke, EE8.3H, 12mH
4	1	T1	Transformer, EPC-17S, 1.4mH
5	1	C1	E-cap, 10μF, 400V
6	1	C2	E-cap, 6.8μF, 400V
7	2	C11, C12	Solid cap, 220μF, 25V
8	1	CY1	Y-cap, 1nF, 1000V
9	1	Q1	N-CH, FET, 600V, 4A
10	1	Q3	N-CH, D-FET, 500V, 20mA
11	1	BR1	Bridge, 1000V, 1A
12	1	D1	Schottky, 100V, 10A
13	1	D5	1000V, 1A, FR107
14	1	D7	100V, 100mA, 1N4148
15	1	C4	470pF, 250V, 10%, X7R
16	1	C5	1nF, 50V, 10%, X7R
17	1	C6	220pF, 250V, 10%, X7R
18	2	C3, C8	4.7μF, 16V, 10%, X7R
19	1	C7	1μF, 16V, 10%, X7R
20	1	C10	220pF, 50V, 10%, X7R
21	1	R0	270kΩ, 5%, 1/4W
22	1	R1	30kΩ, 1%, 1/8W
23	1	R2	330kΩ, 5%, 1/8W
24	1	R3	100Ω, 5%, 1/8W
25	2	R4, R12	3.2Ω, 1%, 1/8W
26	1	R5	100kΩ, 5%, 1/10W
27	1	R6	500Ω, 5%, 1/10W
28	1	R7	10Ω, 5%, 1/10W
29	1	R8	1kΩ, 5%, 1/10W
30	1	R9	3.57kΩ, 1%, 1/10W
31	1	R10	27.3kΩ, 1%, 1/10W
32	1	R11	1.1Ω, 5%, 1/10W
33	1	R14	22Ω, 5%, 1/8W
34	1	R15	3kΩ, 1%, 1/10W
35	1	TH1	Thermistor, NTC

## 7.0 Transformer Drawing

### Schematic:

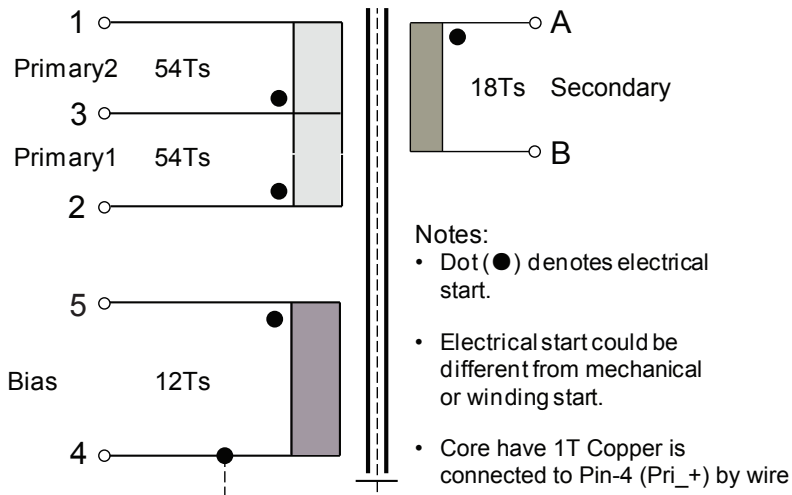

### Electrical Specifications:

1. Primary inductance ( $L_p$ ) =  $1400\mu H \pm 5\%$ @10KHz
2. Primary leakage inductance  $< 5\% * L_p$ , short pin A, pin B
3. Electrical strength = 3KV, 50/60Hz, 1min

### Materials:

1. Core: EPC17S (Ferrite Material JP95)
2. Bobbin: EPC17S, Vertical
3. Magnet Wires (Pri): Type 2-UEW
4. Magnet Wire (Sec): Triple Insulated Wires
5. Layer Insulation Tape: 3M1298 or equivalent

### Finished:

1. Varnish the complete assembly
2. Cut pin 3

## 8.0 Performance


### 8.1 Regulation, Ripple and Efficiency Measurement

\* Note: All data measured at cable end with 10 $\mu$ F E-cap and 1 $\mu$ F ceramic cap at cable end. Scope bandwidth is set at 20MHz.


Cable length is 3 feet (flat cable), cable resistance is at 220m ohm,

Vin (V <sub>AC</sub> )	Pin (W)	Vout (V)	Iout (mA)	V <sub>ripple</sub> (mV <sub>P-P</sub> )	Pout (W)	$\eta$ (%)	OCP (A)	Average $\eta$ (%)
90	0.03	20.01	0	28			0.72	85.73
	3.48	19.93	0.15	60	2.99	85.91		
	6.90	19.92	0.3	92	5.98	86.61		
	10.43	19.95	0.45	104	8.98	86.07		
	14.22	19.99	0.6	226	11.99	84.35		
120	0.032	20.01	0	30			0.79	86.61
	3.47	19.93	0.15	72	2.99	86.15		
	6.84	19.92	0.3	122	5.98	87.37		
	10.36	19.95	0.45	112	8.98	86.66		
	13.90	19.98	0.6	120	11.99	86.24		
230	0.040	19.99	0	34			0.79	86.27
	3.52	19.92	0.15	64	2.99	84.89		
	6.90	19.85	0.3	102	5.96	86.30		
	10.30	19.93	0.45	116	8.97	87.07		
	13.80	19.97	0.6	114	11.98	86.83		
265	0.040	20.01	0	36			0.79	85.24
	3.60	19.95	0.15	70	2.99	83.13		
	7.00	19.92	0.3	90	5.98	85.37		
	10.40	19.94	0.45	96	8.97	86.28		
	13.90	19.97	0.6	120	11.98	86.20		

### 8.2 Conducted EMI

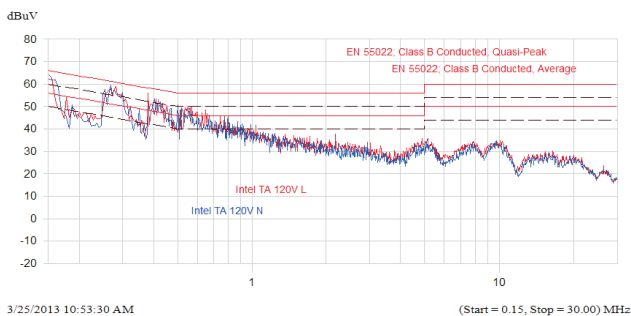

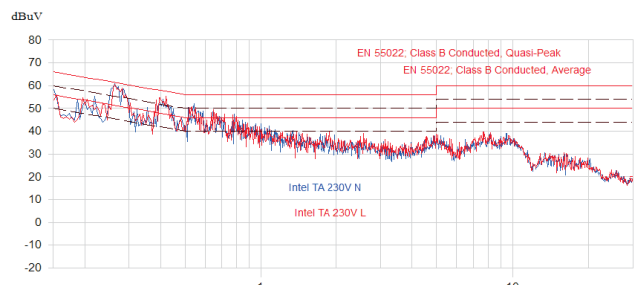Peak scan @ 120V<sub>AC</sub> output-short to GND



Peak scan @ 230V<sub>AC</sub> output-short to GND



## Disclaimer

Information in this document is believed to be accurate and reliable. However, Dialog Semiconductor does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information. Dialog Semiconductor furthermore takes no responsibility whatsoever for the content in this document if provided by any information source outside of Dialog Semiconductor.

Dialog Semiconductor reserves the right to change without notice the information published in this document, including without limitation the specification and the design of the related semiconductor products, software and applications.

Applications, software, and semiconductor products described in this document are for illustrative purposes only. Dialog Semiconductor makes no representation or warranty that such applications, software and semiconductor products will be suitable for the specified use without further testing or modification. Unless otherwise agreed in writing, such testing or modification is the sole responsibility of the customer and Dialog Semiconductor excludes all liability in this respect.

Customer notes that nothing in this document may be construed as a license for customer to use the Dialog Semiconductor products, software and applications referred to in this document. Such license must be separately sought by customer with Dialog Semiconductor.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

DIALOG SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of Dialog Semiconductor products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to Dialog Semiconductor.

Dialog's semiconductors are typically used in power supplies in which high voltages are present during operation. High-voltage safety precautions should be observed in design and operation to minimize the chance of injury.

All use of Dialog Semiconductor products, software and applications referred to in this document are subject to Dialog Semiconductor's [Standard Terms and Conditions of Sale](#), unless otherwise stated.

PrimAccurate is a registered trademark of iWatt Inc., an affiliated company of Dialog Semiconductor plc. Dialog and the Dialog logo are trademarks of Dialog Semiconductor plc. Intel and Ultrabook are trademarks of Intel Corporation in the U.S. and/or other countries.

© Dialog Semiconductor GmbH. All rights reserved.

## RoHS Compliance

Dialog Semiconductor complies to Directive 2002/95/EC of the European Parliament and of the Council of 27 January 2003 concerning Restriction of Hazardous Substances (RoHS). Dialog Semiconductor's statement on RoHS can be found on the customer portal <https://support.diasemi.com/> RoHS certificates from our suppliers are available on request.



Dialog Semiconductor North America  
Power Conversion Business Group  
675 Campbell Technology Parkway  
Campbell CA 95008 USA

[www.iwatt.com](http://www.iwatt.com)  
[info@iwatt.com](mailto:info@iwatt.com)  
+1 (408) 374-4200

[www.iwatt.com](http://www.iwatt.com)

