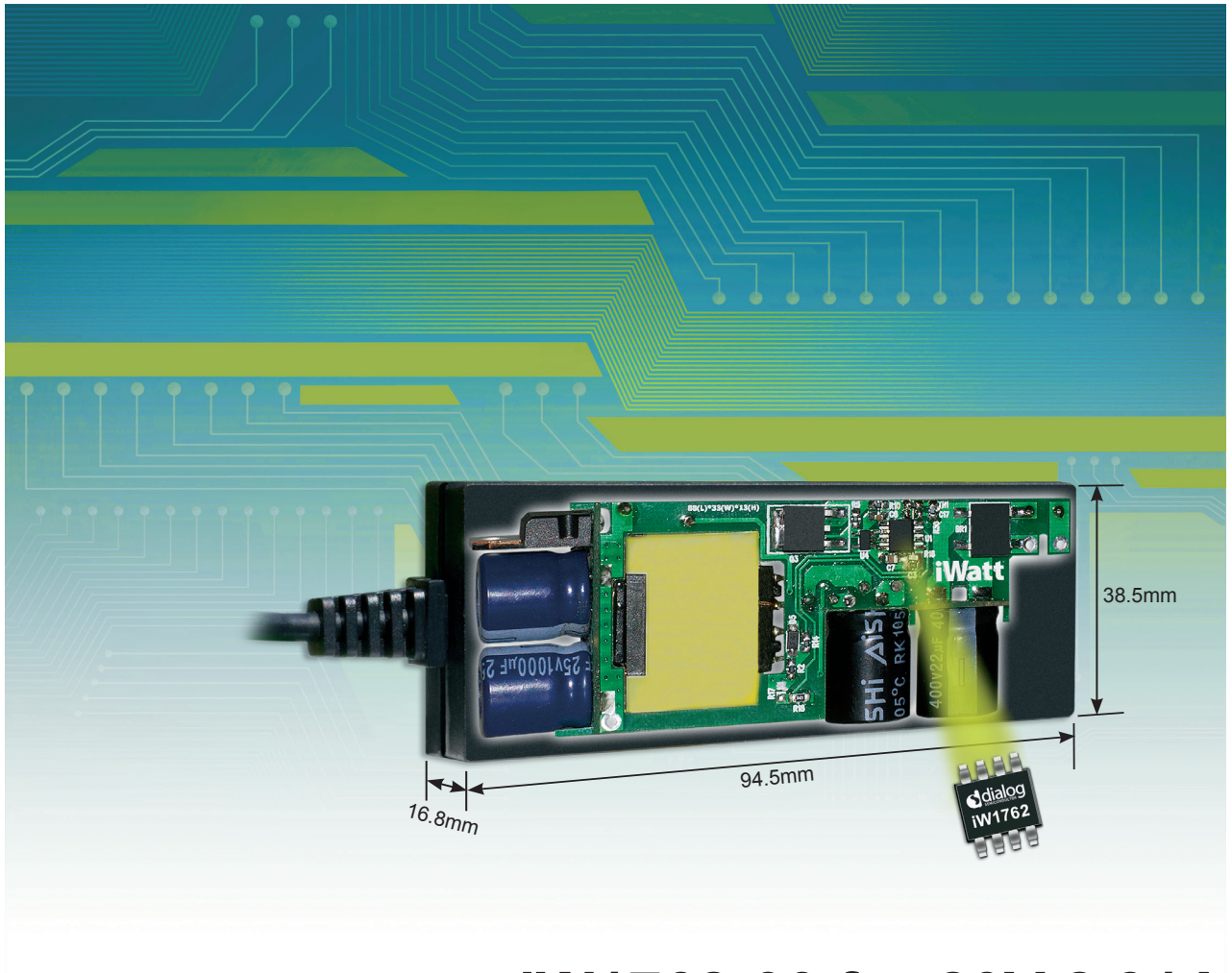


Reference Design

EBC10061



**iW1762-00 for 20V 2.31A
Ultra-Slim 45W Ultrabook™ Adapter Design**

iW1762-00 for Ultra-Slim 45W Ultrabook™ Adapter Design

(AC Input 90 - 264V_{AC} Output 20V 2.31A)

EBC10061

1.0. Introduction	3
2.0. Design Features	3
3.0. Design Specification	4
4.0. Schematic	5
5.0. PCB Layout.....	5
6.0. Bill of Materials	6
7.0. Transformer Drawing	8
8.0. Performance	8
8.1. Regulation, Ripple and Efficiency	9
8.2. Output VI Characteristics	9
8.3. Conducted EMI	10

1.0 Introduction

This document provides a reference design for a universal input, 20V 2.31A isolated flyback power supply for ultra-slim, 45W ultrabook adapters. This design uses the iW1762-00. This document contains the complete specification for the power supply, a detailed circuit diagram, an entire bill of materials required to build the power supply, a drawing of the power transformer, and test data of the most important performance.



Figure 1.1 PCB Top View

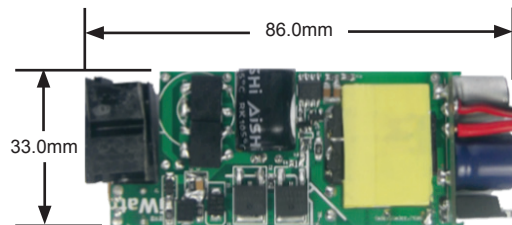


Figure 1.2 PCB Bottom View



Figure 1.3 PCB Side View

2.0 Design Features

- AC input range: 90 – 264V_{AC}
- DC output: 20V, 2.31A
- 82W peak power for 1ms every 10ms
 - » Supports Intel Turbo Boost mode
- < 100mW no-load standby power consumption
- Maximum ripple voltage < 380mV_{P-P}
- PrimAccurate™ primary-side sensing
 - » Eliminates opto-isolator
 - » Reduces BOM
 - » Improves line voltage surge protection
- Tight over voltage protection

3.0 Design Specification

The table below represents the minimum acceptable performance of the design.

Description	Symbol	Min	Typ	Max	Units	Comment
Input						
Voltage	V_{IN}	90		264	V_{AC}	2 Wire
Frequency	f_{LINE}	47	50/60	63	Hz	
No-load input power (230V _{AC})				100	mW	
Output						
Output voltage	V_{OUT_CV}	19	20	21	V	Measured at PCB end of output cable
Output current	I_{OUT_CV}		2.31		A	
Output ripple voltage	V_{RIPPLE}			380	mV _{P-P}	Add 0.1uF Ceramic capacitor and 1μF E-cap at the end of cable and set oscilloscope at 20MHz bandwidth.
Total Output Power						
Continuous output power	P_{OUT}		46.2		W	
Turbo mode peak power (4.3A 86W)			82		W	82W (turbo mode) for 1ms every 10ms
Over-current protection	I_{OUT_MAX}			3.0	A	Auto-restart
Active mode efficiency	η	88			%	Measured at end of PCB $V_{IN}=115V_{AC}$ and 230V _{AC} ($T_{AMB}=25^{\circ}C$)
Environmental						
Conducted EMI		Meets CISPR22B/EN55022B				
Safety		Designed to meet IEC950, UL1950 Class II				
Ambient temperature	T_{AMB}	0		40	°C	Free convection, sea level

4.0 Schematic

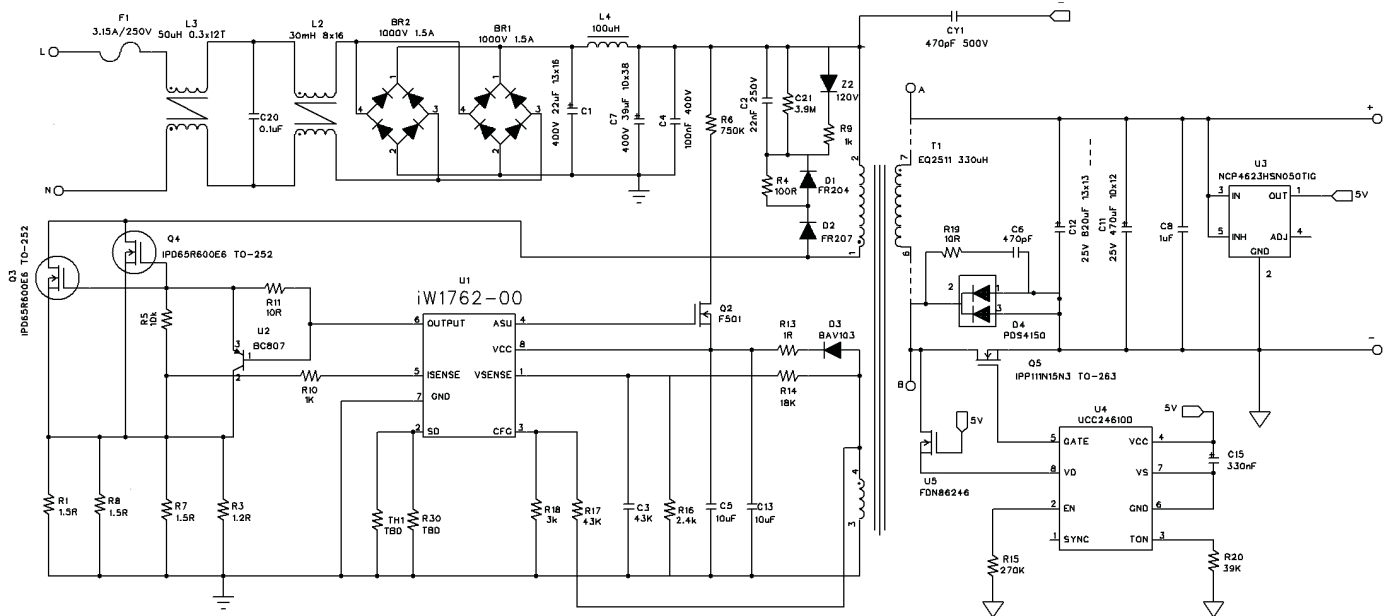


Figure 4.1 Design Schematic

5.0 PCB Layout

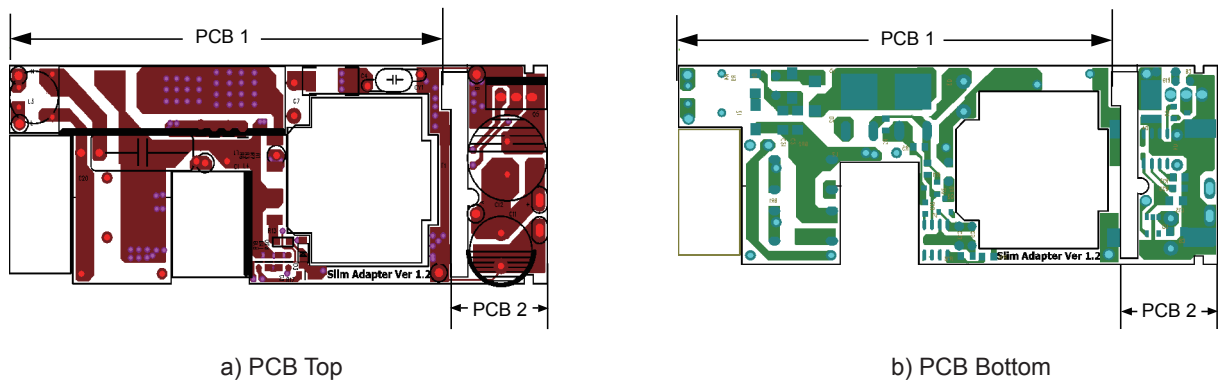


Figure 5.1 PCB Layout. Assembled PCB Layout is 86mm x 33mm x 13mm

6.0 Bill of Materials


Item	Qty.	Ref.	Description
Primary-Side Components			
1	1	U1	iW1762-00, Off-line Digital PSR & PWM & VMS Controller, SOIC-8
2	1	U2	BC807-40, -0.5A/-50V, PNP Transistor, SOT-23
3	1	C1	22μF, 400V, Low-ESR E-Cap, Φ13mm X 16mm Aishi
4	1	C2	22nF, 250V, X7R, SMD-1206
5	1	C4	100nF, 400V SMD
6	2	C5,C13	10μF, 25V, X7R, SMD-1206
7	1	C7	39μF, 400V, Low-ESR E-Cap, Φ10mm X 39mm Aishi
8	1	C20	X-CAP, 0.1μF, 275V
9	2	BR1,BR2	DF10S,1.5A1000V, Rectifier Bridge Fairchild
10	1	D1	FR204, 2A250V
11	1	D2	FR207 2A, 100V
12	1	D3	BAV103, 0.2A250V,Rectifier Diode, LL-34
13	1	Z2	BZD17C120P, 120V 0.8W (25°C), Zener Diodes, DO-219AB (SMF) Vishay
14	1	F1	T 3.15A250V, BOX Fuse
15	1	L2	T14*8*7 0.4*65Ts L>30mH
16	1	L3	T9*5*3 0.35*11Ts L>40uH B29
17	1	L4	100μH, DM-inductor, Core: DR-5mmX10mm*1P, Wire: 0.32mmX85Ts
18	1	Q2	DMZ6005, 12mA600V, Depletion Mode MOSFET, SOT23-3
19	2	Q3,Q4	IPS65R600E6,7.3A700V, Cool-MOSFET, TO-252
20	2	R1,R7,R8	1.5Ω ±1%, SMD-1206
21	1	C21	3.9MΩ ±5%, SMD-1206
22	1	R3	1.2Ω ±1%, SMD-1206
23	1	R4	100Ω ±5%, SMD-1206
24	1	R5	10KΩ ±5%, SMD-0805
25	1	R6	750KΩ ±5%, SMD-1206
26	1	R9	1KΩ ±5%, SMD-1206
27	1	R10	1KΩ ±5%, SMD-0603
28	1	R11	10Ω ±5%, SMD-0603
29	2	R12,R17	43KΩ ±1%, SMD-0603
30	1	R13	1Ω ±5%, SMD-0603
31	1	R14	18KΩ ±1%, SMD-0603
32	1	R16	2.4KΩ ±1%, SMD-0603
33	1	R18	3KΩ ±5%, SMD-0603
34	2	TH1,R30	Optional

6.0 Bill of Materials (continued)

Item	Qty.	Ref.	Description
Secondary-Side Components			
35	1	C6	470pF, 250V, X7R, SMD-0805
36	1	C8	1μF, 50V, X7R, SMD-0805
37	1	C11	470μF, 25V, Solider Capacitor, 10mm*12.5mm
38	1	C12	820μF, 25V, E-Cap, 12.5mm*13mm
39	1	C15	330nF, 6.3V, X7R, SMD-0805
40	1	D4	PDS4150, 4A150V, Schottky Diode, SMD, TO-277A
41	1	Q5	IPI075N15N3, 100A/150V, 7.5mR, TO-263
42	1	U3	NCP4623HSN050TIG, LDO, SOT-23-3
43	1	U4	UCC24610D, SR Controler, SO-8 Package
44	1	U5	FDN86246, N-Channel power, 150V/1.6A/0.261mR
45	1	R15	270KΩ ±5%, SMD-0603
46	1	R19	10Ω ±5%, SMD-0805
47	1	R20	39KΩ ±1%, SMD-0603
48	1	Y Cap	Y1 Cap, 470pF
Other Components			
49	1	T1	EQ2511, Lp=330μH±5%
50	1	PCB	Double Layer Board, 94V0, FR-4, 1.0mm
51	2	L,N connecting line	OD: 0.3mm, L=15mm
52	1	AL Shielding CASE	AL 180mm*76mm*0.3mm

7.0 Transformer Drawing

Schematic:

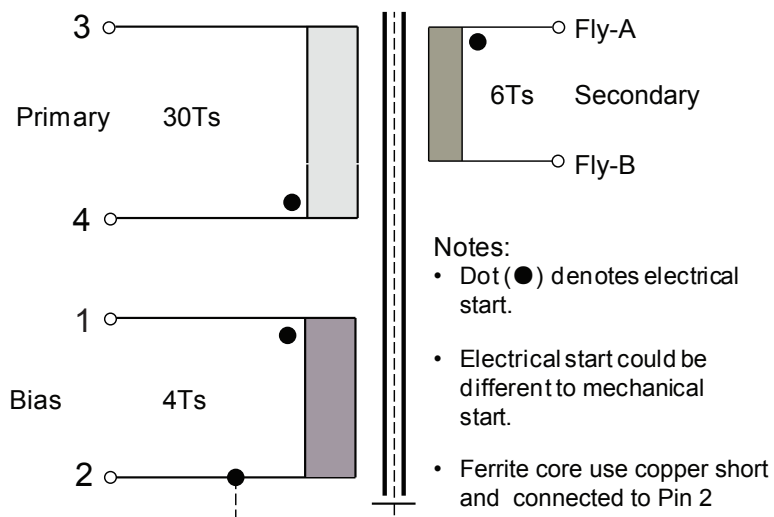

Electrical Specifications:

1. Primary inductance (L_p) = $330\mu H \pm 5\%$ @10KHz/1.0V
2. Primary leakage inductance $< 5\% * L_p$, short Fly-A, Fly-B
3. Electrical strength = 3KV, 50/60Hz, 1min

Materials:

1. Core: EQ2511(ferrite material TDK PC40 or equivalent)
2. Bobbin: 4 pins, EQ2511
3. Magnet wires: type 2-UEW
4. Primary wires: 2-UEW
5. Layer insulation tape: 3M1298 or equivalent

Finished:

1. Varnish the complete assembly

8.0 Performance

8.1 Regulation, Ripple and Efficiency Measurement

* Note: Output voltage is measured at end of PCB

Vin (V _{AC})	Pin (W)	Vout (V)	Iout (mA)	V _{ripple} (mV _{P-P})	Pout (W)	η (%)	OCP (A)	Average η (%)	DoE η(%)
90	0.066	20.01	0	13			2.85	90.04	88.0
	12.790	19.75	0.575	76	11.36	88.79			
	25.100	19.80	1.15	180	22.77	90.72			
	37.840	19.92	1.725	140	34.36	90.81			
	51.480	20.02	2.31	270	46.25	89.83			
115	0.070	19.98	0	15			2.83	90.71	
	12.750	19.75	0.575	61	11.36	89.07			
	25.080	19.77	1.15	220	22.74	90.65			
	37.480	19.93	1.725	210	34.38	91.73			
	50.630	20.03	2.31	220	46.27	91.39			
230	0.074	20.00	0	14			2.82	91.31	
	12.560	19.77	0.575	87	11.37	90.51			
	25.280	19.80	1.15	80	22.77	90.07			
	37.250	19.91	1.725	230	34.34	92.20			
	50.050	20.03	2.31	190	46.27	92.45			
264	0.094	20.00	0	15			2.79	90.66	
	12.680	19.76	0.575	110	11.36	89.61			
	25.640	19.83	1.15	102	22.80	88.94			
	37.410	19.92	1.725	150	34.36	91.85			
	50.170	20.03	2.31	215	46.27	92.23			

8.2 Output VI Characteristics


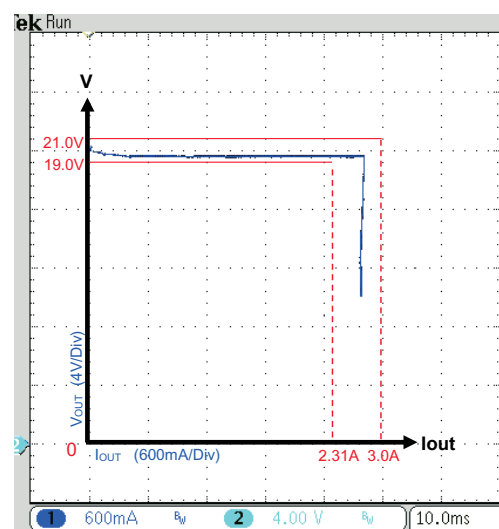
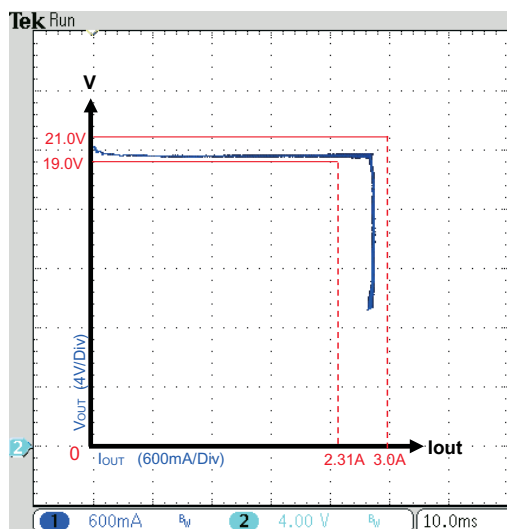



Figure 8.2 Output VI Characteristics

8.0 Performance (continued)

8.3 Conducted EMI

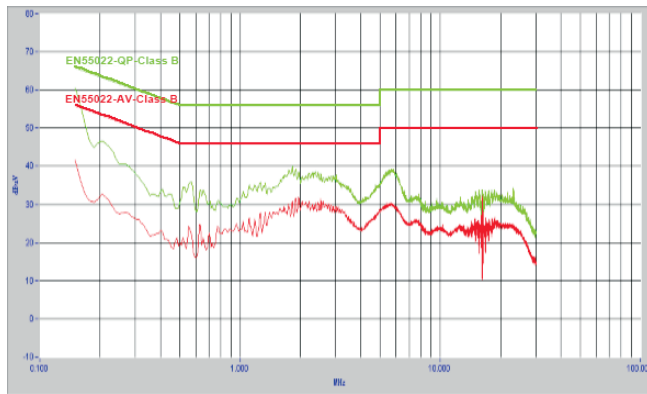


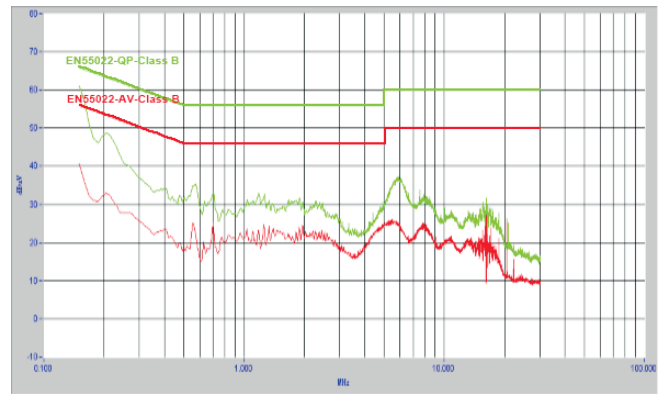a) $V_{IN}=230V_{AC}/50Hz$, QP & AV Scan L




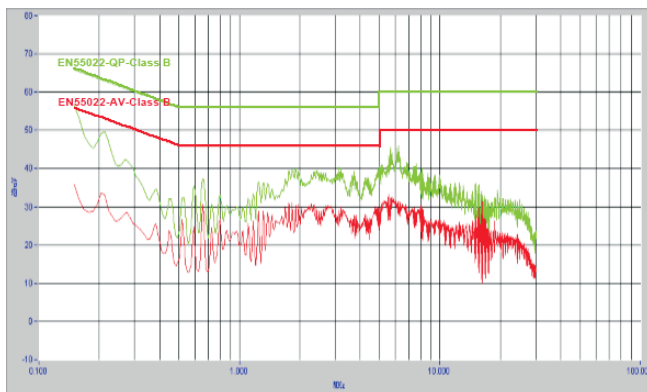b) $V_{IN}=230V_{AC}/50Hz$, QP & AV Scan N

* Note: The UUT is full load (8.4Ω), output (-) is floating.



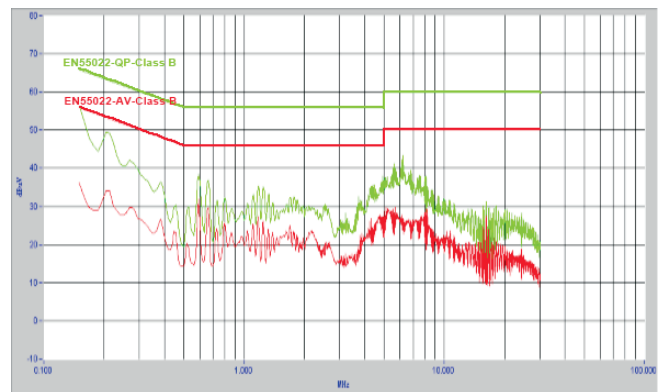c) $V_{IN}=230V_{AC}/50Hz$, QP & AV Scan L



d) $V_{IN}=230V_{AC}/50Hz$, QP & AV Scan N

* Note: The UUT is full load (8.4Ω), output (-) is connected to earth.

Figure 8.3 EMI Results



Disclaimer

Information in this document is believed to be accurate and reliable. However, Dialog Semiconductor does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information. Dialog Semiconductor furthermore takes no responsibility whatsoever for the content in this document if provided by any information source outside of Dialog Semiconductor.

Dialog Semiconductor reserves the right to change without notice the information published in this document, including without limitation the specification and the design of the related semiconductor products, software and applications.

Applications, software, and semiconductor products described in this document are for illustrative purposes only. Dialog Semiconductor makes no representation or warranty that such applications, software and semiconductor products will be suitable for the specified use without further testing or modification. Unless otherwise agreed in writing, such testing or modification is the sole responsibility of the customer and Dialog Semiconductor excludes all liability in this respect.

Customer notes that nothing in this document may be construed as a license for customer to use the Dialog Semiconductor products, software and applications referred to in this document. Such license must be separately sought by customer with Dialog Semiconductor.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

DIALOG SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of Dialog Semiconductor products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to Dialog Semiconductor.

Dialog's semiconductors are typically used in power supplies in which high voltages are present during operation. High-voltage safety precautions should be observed in design and operation to minimize the chance of injury.

All use of Dialog Semiconductor products, software and applications referred to in this document are subject to Dialog Semiconductor's [Standard Terms and Conditions of Sale](#), unless otherwise stated.

PrimAccurate is a registered trademark of iWatt Inc., an affiliated company of Dialog Semiconductor plc. Dialog and the Dialog logo are trademarks of Dialog Semiconductor plc. Intel and Ultrabook are trademarks of Intel Corporation in the U.S. and/or other countries.

© Dialog Semiconductor GmbH. All rights reserved.

RoHS Compliance

Dialog Semiconductor complies to Directive 2002/95/EC of the European Parliament and of the Council of 27 January 2003 concerning Restriction of Hazardous Substances (RoHS). Dialog Semiconductor's statement on RoHS can be found on the customer portal <https://support.diasemi.com/> RoHS certificates from our suppliers are available on request.



Dialog Semiconductor North America
Power Conversion Business Group
675 Campbell Technology Parkway
Campbell CA 95008 USA

www.iwatt.com
info@iwatt.com
+1 (408) 374-4200

www.iwatt.com

